
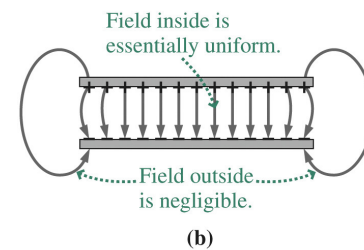


© 2012 Pearson Education, Inc.

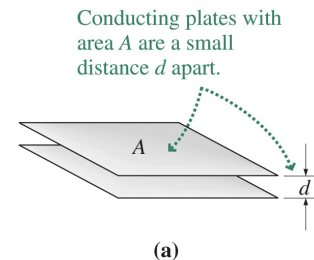

© 2012 Pearson Education, Inc.

University Physics 227N/232N

Capacitors, Field Energy, Current and Ohm's Law

Lab deferred to Fri Feb 28

QUIZ this Friday! (Feb 21) Fred lectures Monday! (Feb 24)

Dr. Todd Satogata (ODU/Jefferson Lab)

satogata@jlab.org

<http://www.toddsatogata.net/2014-ODU>

Wednesday, February 19 2014

Happy Birthday to Victoria Justice, Immortal Technique, Benicio del Toro,
Copernicus, and David Gross (2004 Nobel Prize)



Jefferson Lab

Prof. Satogata / Spring 2014 ODU University Physics 227N/232N 1



Capacitor Review

- A **capacitor** is a pair of conductors, insulated from each other, and used to **store charge and energy**.
 - The two conductors are given equal but opposite charges $\pm Q$
 - Definition of capacitance: $C \equiv Q/V$ $Q = CV$
 - Capacitance is a **physical property** of the capacitor.
- A **parallel plate capacitor** has two parallel conductors of equal area A separated by distance d , possibly a **dielectric**

$$C_{\text{parallel plate}} = \kappa \frac{A}{4\pi k d} = \kappa C_0 \quad C_0 = \frac{A}{4\pi k d} \quad \kappa \geq 1$$

- The dielectric constant κ for a vacuum is 1
- Energy stored in a capacitor


$$U_{\text{stored in capacitor}} = \frac{1}{2} CV^2 = \frac{1}{2} QV = \frac{1}{2} \frac{Q^2}{C}$$



Capacitor Example

$$C \equiv Q/V \quad Q = CV$$
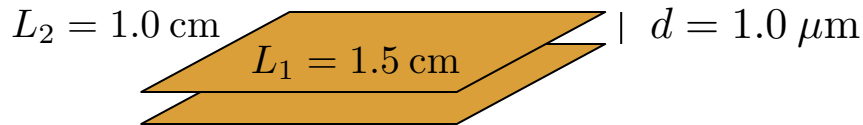
$$C_{\text{parallel plates}} = \frac{\epsilon_0 A}{d} = \frac{A}{4\pi k d}$$



- A (vacuum) capacitor is made of two (parallel) plates of sides 1.5 cm and 1.0 cm separated by 1.0 μm .
 - What is its capacitance?
 - If it is rated at 1 kV, how much charge can it store?

$$C = \frac{A}{4\pi k d} = \frac{1.5 \times 10^{-4} \text{ m}^2}{4\pi(9 \times 10^9 \text{ N m}^2/\text{C}^2)(10^{-6} \text{ m})} = \boxed{1.3 \text{ nF} = C}$$

$$Q = CV = (1.3 \times 10^{-9} \text{ F})(10^3 \text{ V}) = \boxed{1.3 \mu\text{C} = Q}$$

- If we wanted to raise the capacitance, we would need to *increase* the surface area A or *decrease* the separation d
 - Or change the material between the plates



Dielectric Constants

- The **dielectric constant**, κ , is a property of the dielectric material that gives the reduction in field and thus the increase in capacitance.
- For a parallel-plate capacitor with a dielectric between its plates, the capacitance is

$$C = \kappa \frac{\epsilon_0 A}{d} = \kappa C_0 \quad C_0 = \frac{\epsilon_0 A}{d} \quad \kappa \geq 1$$

Table 23.1 Properties of Some Common Dielectrics

Dielectric Material	Dielectric Constant	Breakdown Field (MV/m)
Air	1.0006	3
Aluminum oxide	8.4	670
Glass (Pyrex)	5.6	14
Paper	3.5	14
Plexiglas	3.4	40
Polyethylene	2.3	50
Polystyrene	2.6	25
Quartz	3.8	8
Tantalum oxide	26	500
Teflon	2.1	60
Water	80	depends on time and purity

Titanium dioxide $\kappa=100!$

But breakdown fields
Only up to about 50 MV/m




Connecting Capacitors in Parallel

- Capacitors connected in **parallel** have their top plates connected together and their bottom plates connected together.
 - Therefore the potential difference ΔV across the two capacitors (between the conductive wires on either side) is the same.
 - The capacitance of the combination is the sum of the capacitances:


$$C_{\text{parallel}} = C_1 + C_2 + C_3 + \dots$$

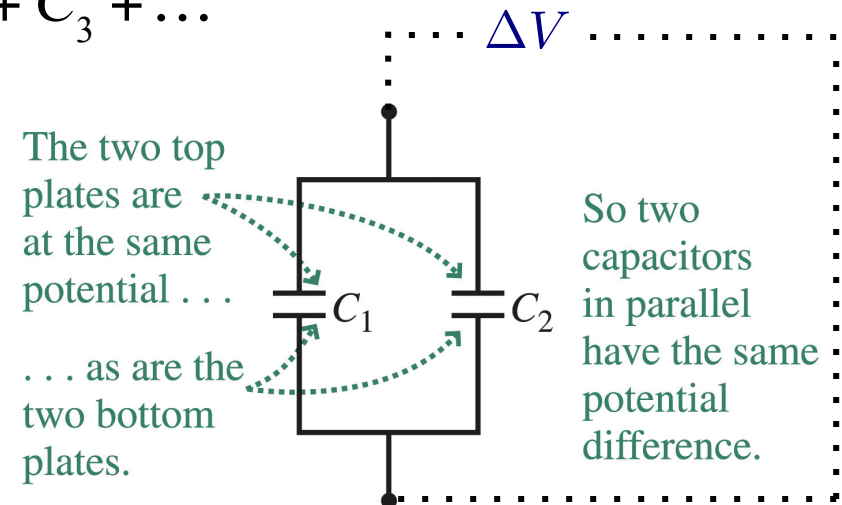- The maximum safe **working voltage** of the combination is that of the capacitor with the lowest voltage rating.



Connecting Capacitors in Parallel

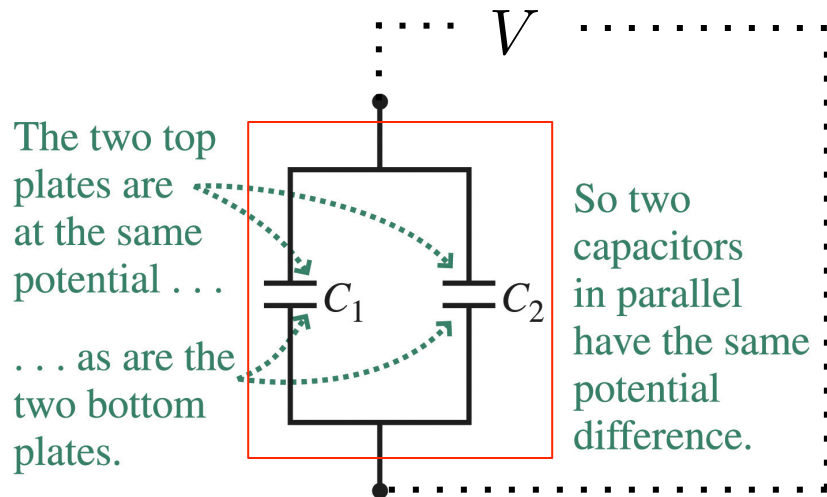We usually just write the voltage difference as V even though it's a difference!
Here the capacitors have the **same potential difference V** .



$$C_1 = \frac{Q_1}{V}$$


$$C_2 = \frac{Q_2}{V}$$

$$Q = Q_1 + Q_2$$

$$C = \frac{Q}{V}$$

$$C = C_1 + C_2$$

Equivalent capacitance

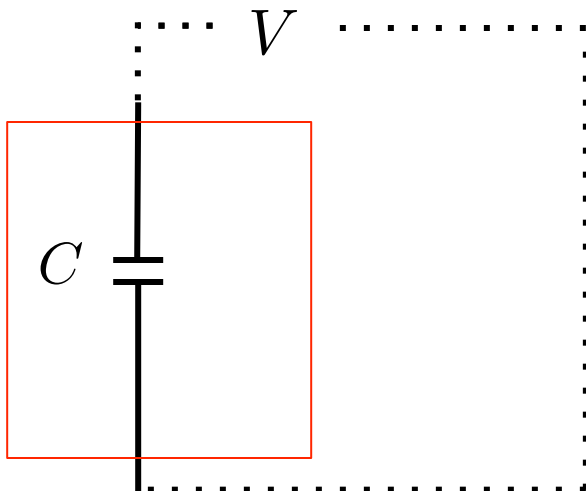

Connecting Capacitors in Series


- Capacitors connected in **series** are wired so that one capacitor follows the other.

- The figure shows that this makes the charge on the two capacitors the same.
- With series capacitors, capacitance adds reciprocally:

$$\frac{1}{C_{\text{series}}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \dots$$

Thus the combined capacitance is lower than that of any individual capacitor.

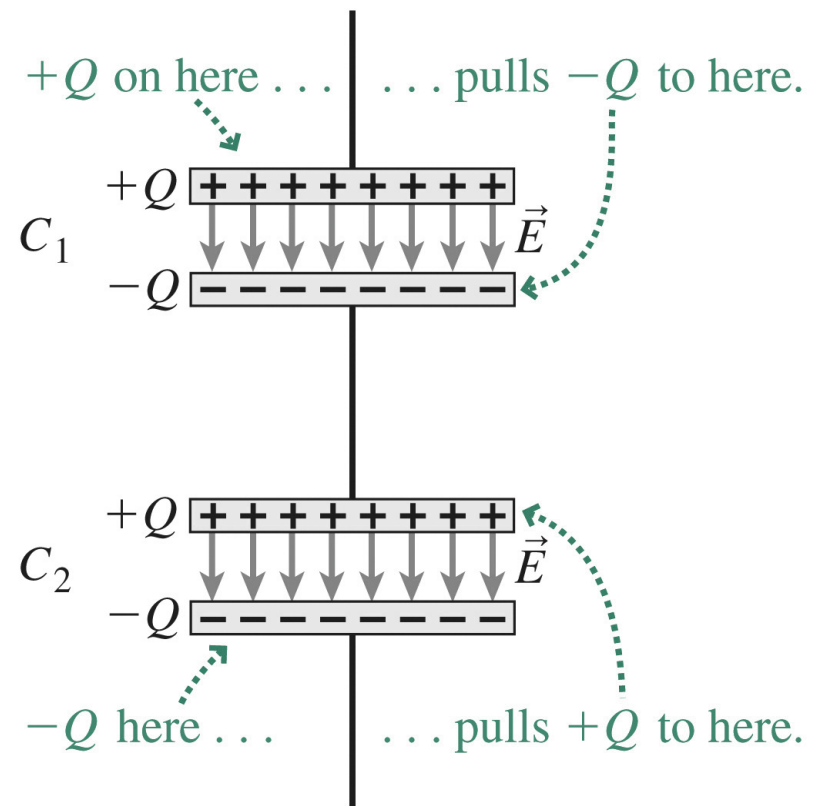- The working voltage of the combination is higher than that of any individual capacitor.




© 2012 Pearson Education, Inc.



Connecting Capacitors in Series

Here the capacitors have the **same charge Q**.

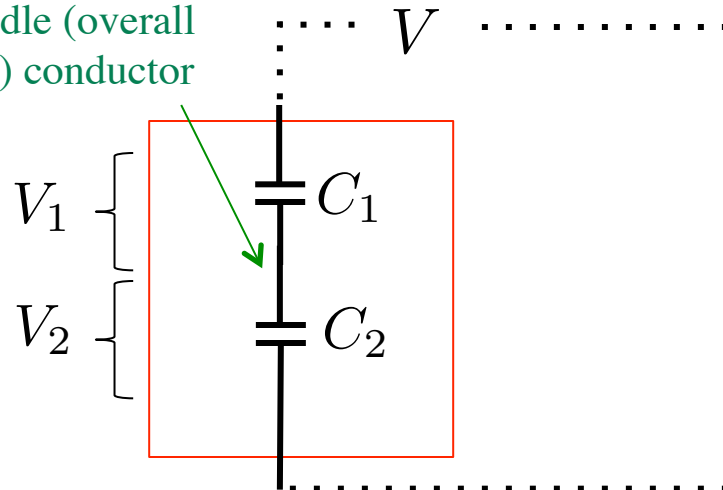Same charges $\pm Q$
on middle (overall
neutral) conductor



$$C_1 = \frac{Q}{V_1}$$

$$C_2 = \frac{Q}{V_2}$$

$$V = V_1 + V_2$$

$$V_1 = \frac{Q}{C_1}$$


$$V_2 = \frac{Q}{C_2}$$

$$\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2}$$

$$V = \frac{Q}{C}$$


$$C = \frac{Q}{V}$$

Equivalent
capacitance

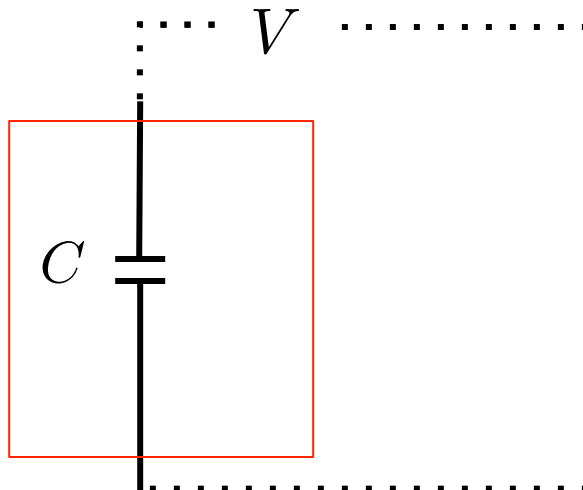


Circuits with Parallel and Series Capacitors

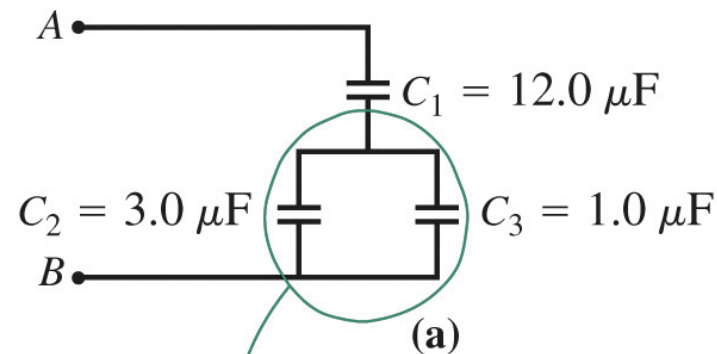
- To analyze a circuit with several capacitors, look for series and parallel combinations.
 - Calculate the equivalent capacitances, and redraw the circuit in simpler form.
 - This technique will work later for more general electric circuits.
- You don't have to draw every single equivalent circuit as long as it's clear to you what you're doing.



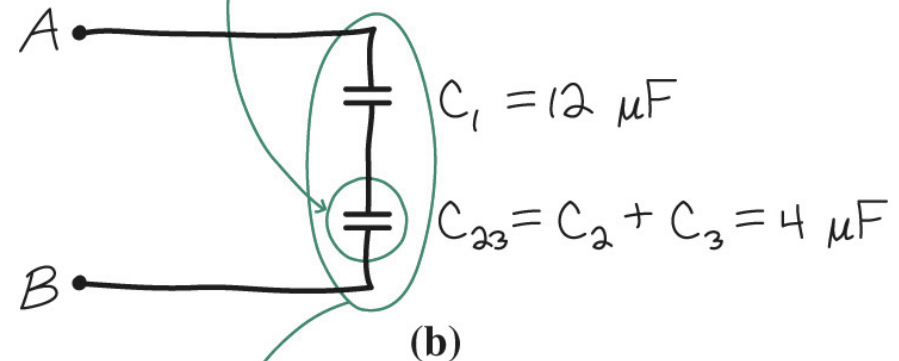C_2 and C_3 form the parallel equivalent C_{23} .



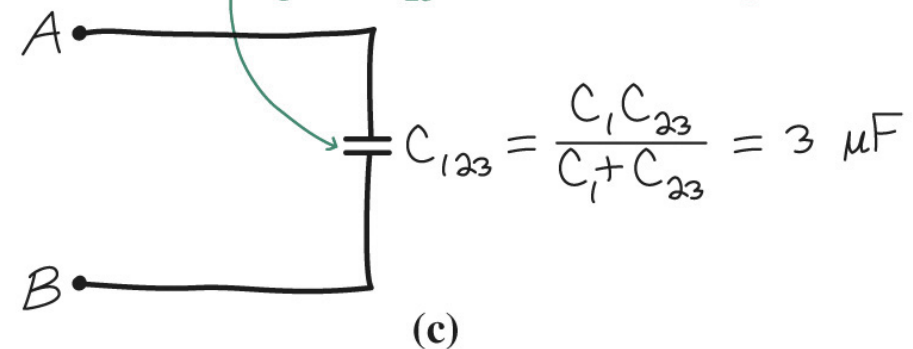
C_1 and C_{23} form the series equivalent C_{123} .



© 2012 Pearson Education, Inc.



Let's Try It Out

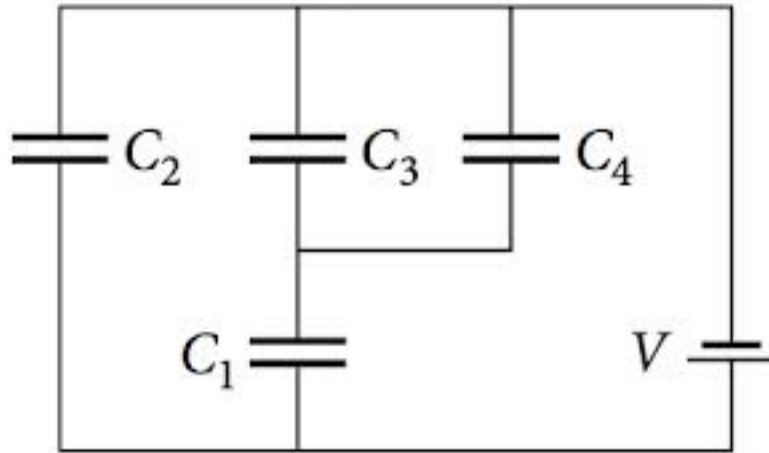


$$C_1 = C_2 = C_3 = C_4 = 4 \mu\text{F}$$

$$V = 30 \text{ V}$$

- Find the equivalent capacitance of the capacitors
- Find the charge on each capacitor



Let's Try It Out: Hint

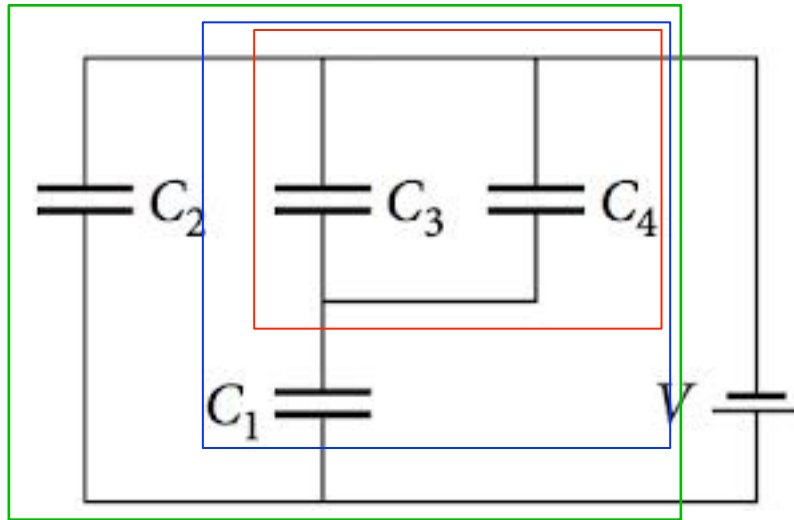

$$C_1 = C_2 = C_3 = C_4 = 4 \mu\text{F}$$


$$V = 30 \text{ V}$$

- Find the equivalent capacitance of the capacitors
- Find the charge on each capacitor
- “Unwrap” the circuit from the inside out
 - Red: two capacitors in parallel
 - Blue: two capacitors (using the above) in series
 - Green: two capacitors (using the above) in parallel



It's Time For Java App Wednesday™
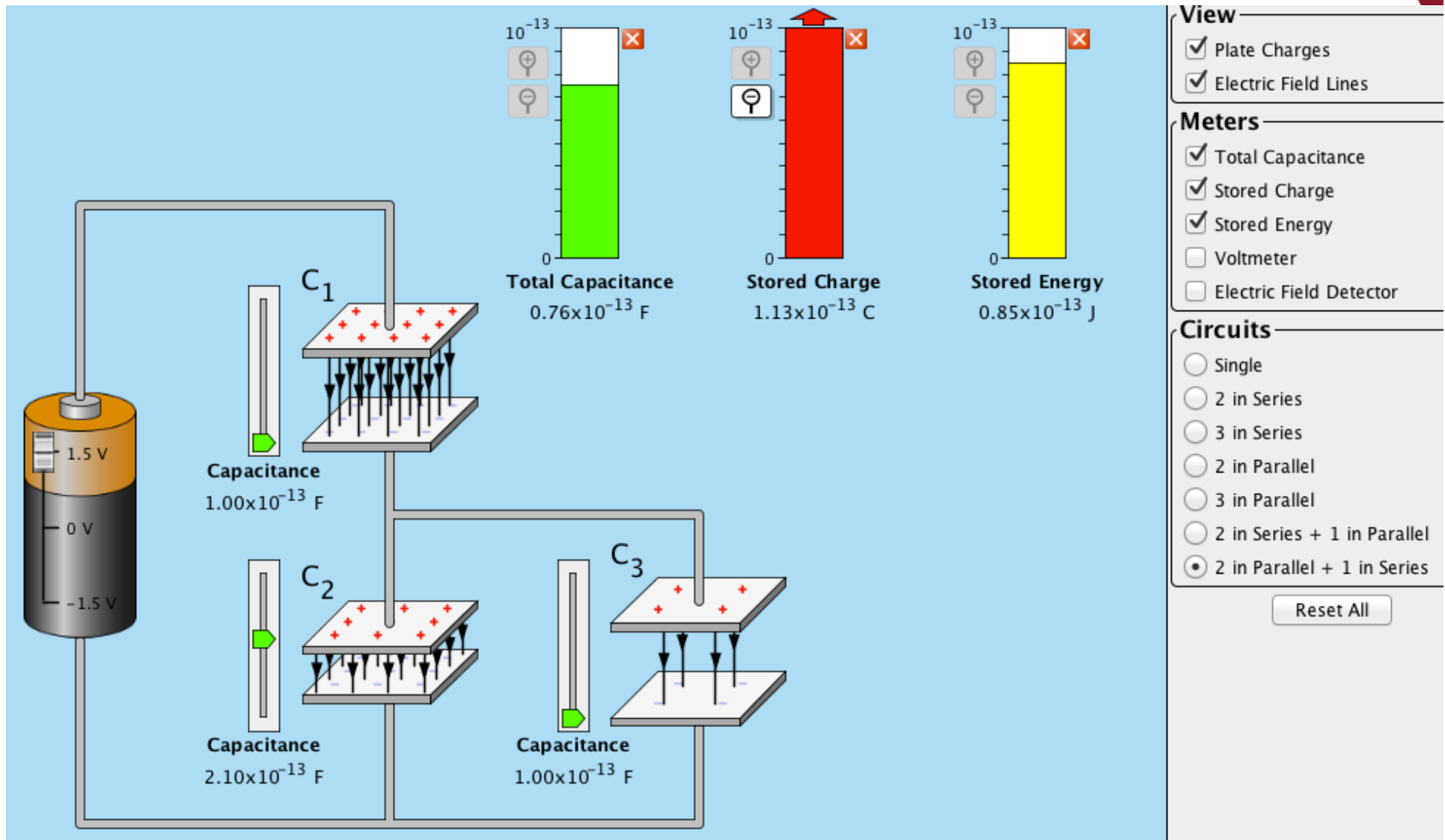
<http://phet.colorado.edu/en/simulation/capacitor-lab>



Energy in the Electric Field


- The electrostatic energy associated with a charge distribution is stored in the electric field of the charge distribution.
 - Considering the uniform field of the parallel-plate capacitor shows that the electric **energy density** is

$$u_E = \frac{E^2}{8\pi k}$$


Energy per unit volume!

- This is a universal result:
 - *Every* electric field contains energy with this density.
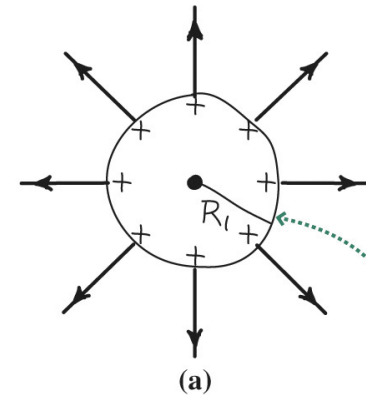
$$U_E \text{ in volume } V = \frac{E^2 V}{8\pi k}$$



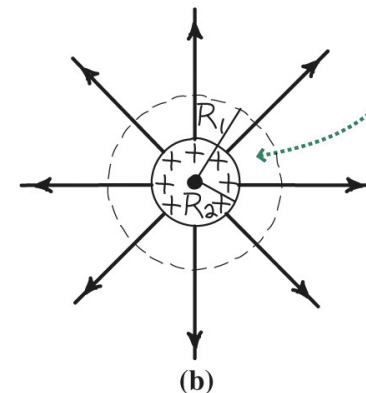The work involved in shrinking the sphere ends up as energy in the electric field here.



© 2012 Pearson Education, Inc.



What's The Electric Field of Sunlight?

- Energy/area at the Earth is about 1350 W/m²
- Let's say sunlight travels at the speed of light, $c=3 \times 10^8$ m/s
- One second of sunlight over one square meter therefore contains about 3×10^8 m³ of sunlight and 1350 J of energy.

$$u = \frac{1350 \text{ J}}{3 \times 10^8 \text{ m}^3} = 4.5 \times 10^{-6} \text{ J/m}^3$$

$$u_E = \frac{E^2}{8\pi k}$$

$$E = \sqrt{8\pi k(4.5 \times 10^{-6} \text{ J/m}^3)} = 1 \text{ kV/m}$$




This is pretty close, but a little high for reasons we'll get to next week.
(The actual answer is still about 800 V/m!)



Chapter 24: Current, Resistors, and Ohm's Law

- “Classical” analog electronic circuits are made from four types of elements
 - Capacitors
 - Electrical energy storage: “springs”
 - Resistors
 - Electrical energy dissipation: “friction”
 - Voltage sources (EMF)
 - Electrical energy (potential difference) sources
 - Conductive wires
 - Treated as perfectly conductive
 - (But we know they really have some small resistance too)
- We characterize electrical circuits with
 - **Voltage** (potential) differences V between various points
 - **Current** (electron) flow I between various points
 - **DC**: Constant current (including zero) **AC**: time-varying current

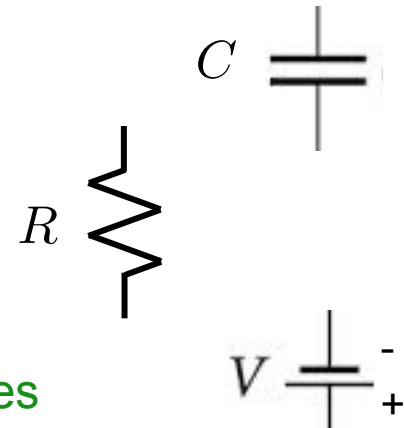


Electric Current

- **Electric current** is a net flow of electric charge.
 - Quantitatively, current is the rate at which charge crosses a given area.

- For steady current, $I = \frac{\Delta Q}{\Delta t}$
- When current varies with time, its instantaneous value is given by


$$I = \frac{dQ}{dt} \quad \text{Ampere} \equiv \frac{\text{Coulomb}}{\text{sec}}$$

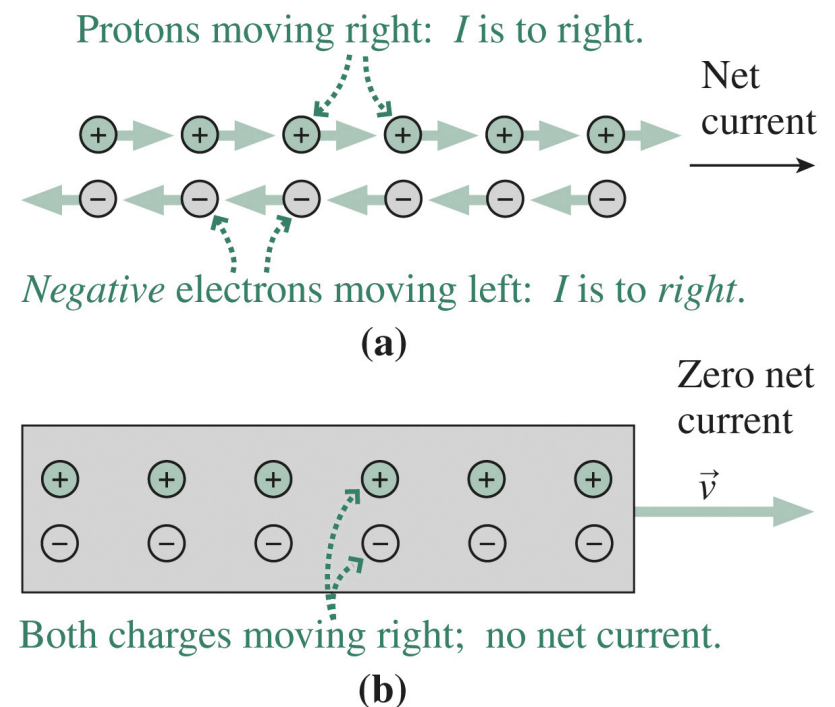- The direction of the current corresponds to the direction of flow of the **positive** charges.
- Current has a **direction**





Conduction Mechanisms

- Conduction occurs differently in different types of materials:
 - In **metallic conductors**, current is carried by free electrons.
 - In **ionic solutions**, current is carried by positive and negative ions.
 - Plasmas** are ionized gases, with current carried by electrons and ions.
 - Semiconductors** involve current carried by both electrons and “holes”—absences of electrons in a crystal structure.
 - Semiconductors are at the heart of modern electronics.
 - Their electrical properties can be altered by the controlled addition of small amounts of impurities.
 - Superconductors** offer zero resistance to the flow of current, and thus can transmit electric power without loss of energy.
 - Known superconducting materials all require temperatures far below typical ambient temperatures.

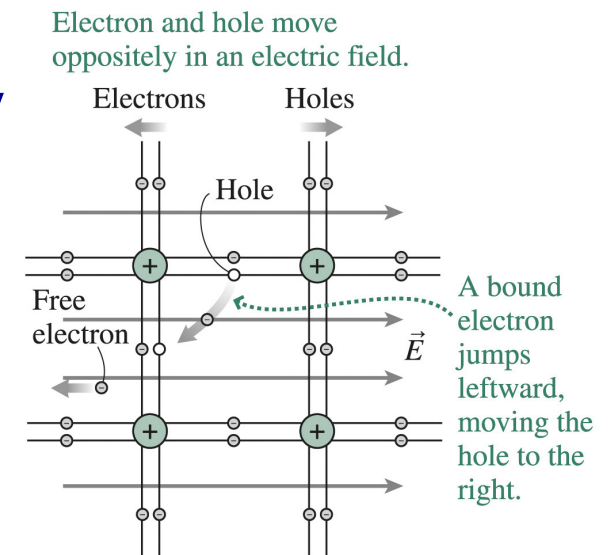

Conduction in Metals

- A **metal** contains a “sea” or “gas” of free electrons:
 - They're confined to the metal (conductor) but not bound to individual atoms.
 - The electrons move about in random directions with high thermal velocities.
 - On *average*, there's no current associated with thermal motion.
 - Applying an electric field adds a small drift velocity on the electrons' motion.
 - All electrons share the drift velocity, so it results in a current.

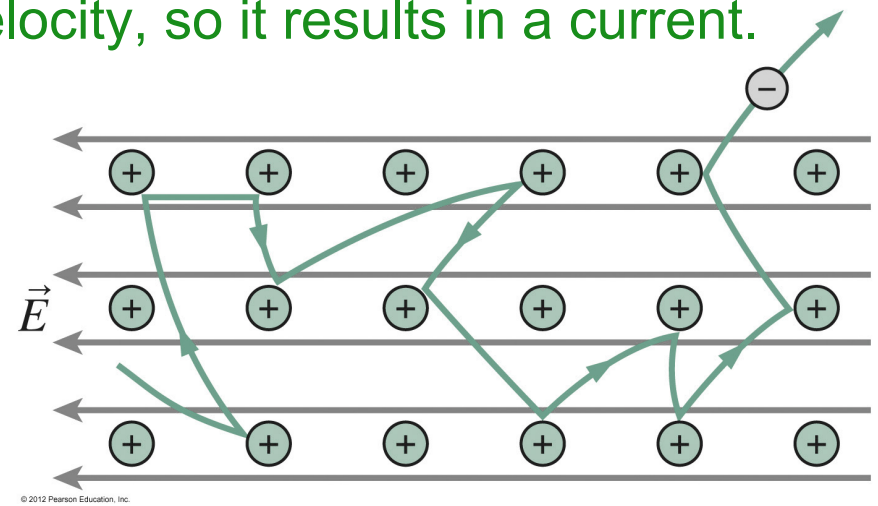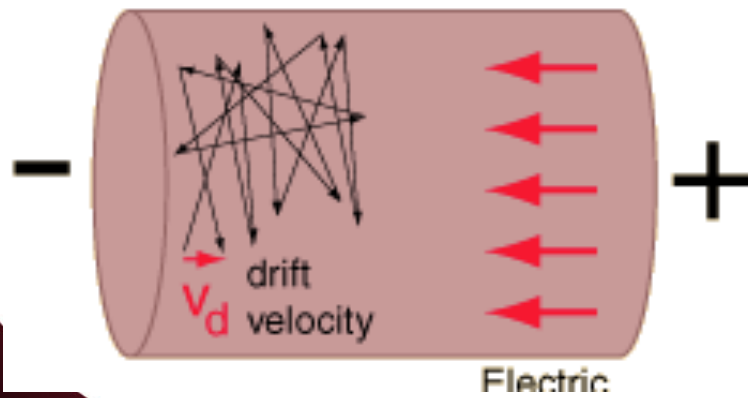

Ohm's Law: Microscopic

- Electrons often collide with ions (nuclei) in the metal's crystal structure
 - They usually lose energy this way
 - This limits how easily the electrons "flow" through the material
- This produces resistance to current flow
 - Quantified as **conductivity** σ of the metal
 - Current per unit area, or current density \vec{J} is then

$$\vec{J} = \sigma \vec{E}$$
 - Resistivity:** $\rho \equiv \frac{1}{\sigma}$

Table 24.1 Resistivities


Material	Resistivity ($\Omega \cdot \text{m}$)
Metallic conductors (20°C)	
Aluminum	2.65×10^{-8}
Copper	1.68×10^{-8}
Gold	2.24×10^{-8}
Iron	9.71×10^{-8}
Mercury	9.84×10^{-7}
Silver	1.59×10^{-8}
Ionic solutions (in water, 18°C)	
1-molar CuSO_4	3.9×10^{-4}
1-molar HCl	1.7×10^{-2}
1-molar NaCl	1.4×10^{-4}
H_2O	2.6×10^5
Blood, human	0.70
Seawater (typical)	0.22
Insulators	
Ceramics	10^{11} – 10^{14}
Glass	10^{10} – 10^{14}
Polystyrene	10^{15} – 10^{17}
Rubber	10^{13} – 10^{16}
Wood (dry)	10^8 – 10^{14}

© 2012 Pearson Education, Inc.



Ohm's "Law" for Resistive Devices

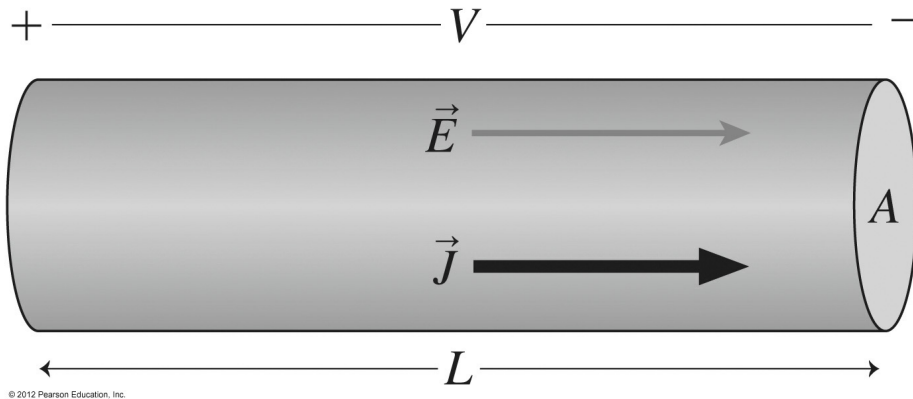- How do we relate this to electric current and voltage?



V : potential difference
 \vec{E} : Electric field
 \vec{J} : Current density
 I : Electric current

- We can calculate a total resistance to current flowing based on the resistivity ρ and physical properties of the resistor

$$R = \frac{\rho L}{A}$$

- A general rule (called a law though it's really not truly a law):

$$V = IR$$

Ohm's "Law"



Ohm's "Law": Microscopic and Macroscopic

Table 24.2 Microscopic and Macroscopic Quantities and Ohm's Law

Microscopic	Macroscopic	Relation
Electric field, \vec{E}	Voltage, V	\vec{E} is defined at each point in a material; V is the integral of \vec{E} over a path. In a uniform field, $V = EL$.
Current density, \vec{J}	Current, I	\vec{J} is defined at each point in a material; I is the integral of \vec{J} over an area. With uniform current density, $I = JA$.
Resistivity, ρ	Resistance, R	ρ is a property of a given material; R is a property of a particular piece of that material. In a piece with uniform cross section, $R = \rho L/A$.
Ohm's law $\vec{J} = \frac{\vec{E}}{\rho}$	Ohm's law $I = \frac{V}{R}$	Microscopic version relates current density to electric field at a point in a material. Macroscopic version relates current through to voltage across a given piece of material.

© 2012 Pearson Education, Inc.

Power Dissipated In A Resistor

- We had a formula for the energy stored in a capacitor

$$U_{\text{stored in capacitor}} = \frac{1}{2}CV^2 = \frac{1}{2}QV = \frac{1}{2}\frac{Q^2}{C} \quad C \equiv \frac{Q}{V}$$

- This is the energy stored in a capacitor at a particular charge
- Now we're considering circuits where charges is moving

$$I = \frac{dQ}{dt}$$

- The power P (energy per unit time!) dissipated by a resistive device with resistance R is

$$P = IV = I^2 R = \frac{V^2}{R} \quad V = IR$$

