

Your name and table number: \_\_\_\_\_

Please show your work, write neatly, write units, and box your answers.

Definition of capacitance:  $C \equiv \kappa Q/V$  where  $\kappa$  is the dielectric constant

Capacitance of a parallel plate capacitor:  $C = A/(4\pi kd)$ ,  $k = 9 \times 10^9 \text{ N m}^2/\text{C}^2$

Capacitors in parallel:  $C_{\text{tot}} = C_1 + C_2 + \dots$

Capacitors in series:  $1/C_{\text{tot}} = 1/C_1 + 1/C_2 + \dots$

1. You build a capacitor out of two parallel thin rectangular conductors, each of length 1.5 cm and width 2.0 cm, separated by a distance of 1.5  $\mu\text{m}$ .

- (a) (2 points) What is its capacitance?

**Solution:** Capacitance of a parallel plate capacitor is  $C = A/(4\pi kd)$ . Here the area of these rectangular conductors is  $A = (0.015 \text{ m})(0.020 \text{ m}) = 3 \times 10^{-4} \text{ m}^2$ . So we have

$$C = \frac{A}{4\pi kd} = \frac{(3 \times 10^{-4} \text{ m}^2)}{4\pi(9 \times 10^9 \text{ N m}^2/\text{C}^2)(1.5 \times 10^{-6} \text{ m})} = 1.768 \text{ nF} \approx \boxed{1.8 \text{ nF} = C}$$

- (b) (2 points) What is the potential difference between the conductors if there is a charge of  $2.0 \times 10^{-7} \text{ C}$  on the capacitor?

**Solution:**  $C \equiv Q/V$ , so

$$V = \frac{Q}{C} = \frac{(2.0 \times 10^{-7} \text{ C})}{(1.768 \times 10^{-9} \text{ F})} = 113 \text{ V} \approx \boxed{110 \text{ V} = V}$$

- (c) (1 point) If you now separate the (charged) plates of the capacitor to a new separation of 4.5  $\mu\text{m}$ , what is the new potential difference between the plates?


**Solution:** The new capacitance of the capacitor is

$$C_{\text{new}} = \frac{A}{4\pi kd_{\text{new}}} = \frac{A}{4\pi kd} \left( \frac{d}{d_{\text{new}}} \right) = C \left( \frac{1}{3} \right)$$

It has the same charge, so the new potential difference (voltage) is

$$V_{\text{new}} = \frac{Q}{C_{\text{new}}} = \frac{(2.0 \times 10^{-7} \text{ C})}{(1.768 \times 10^{-9} \text{ F})(1/3)} = 339 \text{ V} \approx \boxed{340 \text{ V} = V_{\text{new}}}$$

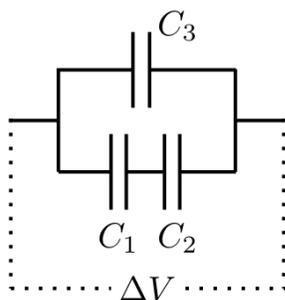The capacitance goes down by a factor of three, so the voltage to hold the same charge must go *up* by a factor of three.



2. Consider the above arrangement of capacitors, where  $C_1 = 2.0 \mu\text{F}$  and  $C_2 = 2.0 \mu\text{F}$  are in series, and  $C_3 = 1.0 \mu\text{F}$  is parallel to the series combination.

- (a) (3 point) What is the overall equivalent capacitance of this combination of capacitors?

**Solution:** Capacitors  $C_1$  and  $C_2$  are in series, so their equivalent capacitance  $C_{12}$  is

$$\frac{1}{C_{12}} = \frac{1}{C_1} + \frac{1}{C_2} = \frac{1}{2.0 \mu\text{F}} + \frac{1}{2.0 \mu\text{F}} = \frac{1}{1.0 \mu\text{F}} \quad \Rightarrow \quad C_{12} = 1.0 \mu\text{F}$$

This equivalent capacitance  $C_{12}$  is in parallel with  $C_3$ , so the total equivalent capacitance  $C_{123}$  is

$$C_{123} = C_{12} + C_3 = (1.0 \mu\text{F}) + (1.0 \mu\text{F}) = \boxed{2.0 \text{ F} = C_{123}}$$

- (b) (2 points) If there is a voltage difference  $\Delta V = 20 \text{ V}$  across this capacitor combination, what is the charge on each capacitor?

**Solution:**  $C_3$  has wires that connect to the terminals of  $\Delta V$ , so the potential difference across  $C_3$  is also  $\Delta V$ . Then we can use the definition of capacitance to find its charge:

$$Q_3 = C_3 \Delta V = (1.0 \mu\text{F})(20 \text{ V}) = \boxed{20 \mu\text{C} = Q_3}$$

We can also use this logic to find the charge on the equivalent capacitance of the series capacitors,  $C_{12}$ :

$$Q_{12} = C_{12} \Delta V = (1.0 \mu\text{F})(20 \text{ V}) = 20 \mu\text{C}$$

How does  $Q_{12}$  relate to the charges on the individual capacitors  $Q_1$  and  $Q_2$ ? The capacitors in series must have the *same* charge. All charge that goes onto the left plate of  $C_1$  is balanced by an equal and opposite charge on the rightmost plate of  $C_1$ . But the central conductor is neutral, so there must also be an equal charge over on the other side of the conductor, on the left plate of  $C_2$ , which is then balanced by an equal and opposite charge on the right plate of  $C_2$ .

The conclusion to all that logic is that the charges  $Q_1$  and  $Q_2$  are both equal to the  $Q_{12}$  you calculated for the equivalent capacitance of the two capacitors in series.

$$\boxed{Q_1 = Q_2 = Q_{12} = 20 \mu\text{C}}$$

Yes, the charges on all three capacitors are the same!