

## Useful Equations

Definition of capacitance:  $C \equiv \frac{Q}{V}$

Capacitance of a parallel plate capacitor:  $C = \kappa \frac{A}{4\pi kd}$  ( $\kappa$ : dielectric constant)

Capacitors in parallel:  $C_{\text{equiv}} = C_1 + C_2 + \dots$

Capacitors in series:  $\frac{1}{C_{\text{equiv}}} = \frac{1}{C_1} + \frac{1}{C_2} + \dots$

Energy stored in capacitor:  $U_{\text{stored}} = \frac{1}{2}CV^2$

Definition of current:  $I \equiv \frac{dQ}{dt}$

Ohm's Law, voltage drop across a resistor:  $V = IR$

Power dissipated by a resistor:  $P = IV = I^2R$  (1 Watt = (1 Coulomb)(1 Volt))

Resistors in series:  $R_{\text{equiv}} = R_1 + R_2 + \dots$

Resistors in parallel:  $\frac{1}{R_{\text{equiv}}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots$

## Useful Geometry Equations

Circle circumference:  $2\pi r$

Circle area:  $\pi r^2$

Sphere surface area:  $4\pi r^2$

Sphere volume:  $\frac{4}{3}\pi r^3$

Cylinder surface area:  $2\pi r^2$  (ends) +  $2\pi rL$  (side)

Cylinder volume:  $\pi r^2L$

## Useful Constants

$k = 9.00 \times 10^9 \text{ N m}^2/\text{C}^2$

$\epsilon_0 = \frac{1}{4\pi k} = 8.85 \times 10^{-12} \text{ C}^2/\text{N m}^2$


1 pF =  $10^{-12}$  F

1 nF =  $10^{-9}$  F

1  $\mu$ F =  $10^{-6}$  F


1 mF =  $10^{-3}$  F

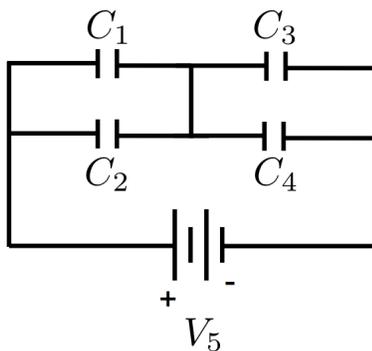Electron charge:  $e = -1.6 \times 10^{-19}$  C



1. The circuit shown above has capacitors  $C_1 = 1.0 \mu\text{F}$ ,  $C_2 = 2.0 \mu\text{F}$ ,  $C_3 = 3.0 \mu\text{F}$ , and  $C_4 = 4.0 \mu\text{F}$  connected by perfectly conducting wires. The EMF  $V_5$  has a voltage across its terminals of  $V_5 = 12.0 \text{ V}$ , and the circuit is in a state where the capacitors are charged.
  - (a) (3 points) Find the equivalent capacitance of the capacitors.
  - (b) (3 points) Find the charges  $Q_1$ ,  $Q_2$ ,  $Q_3$ , and  $Q_4$  of each capacitor.
  - (c) (4 points) Find the voltages  $V_1$ ,  $V_2$ ,  $V_3$ , and  $V_4$  across each capacitor. Are they consistent with the voltage across the EMF?

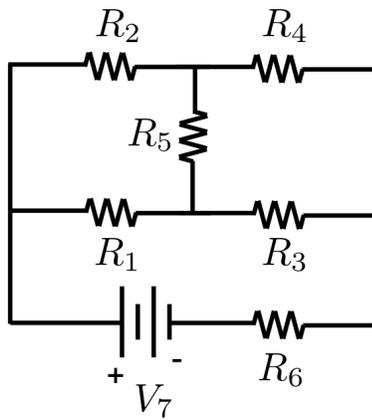2. An incandescent light bulb has a resistance of  $140\ \Omega$  when it is lit and  $9.5\ \Omega$  when it is not lit. It is plugged into a DC power supply that provides a constant voltage of  $120\text{V}$ .
- (a) (2 points) What current goes through the bulb just as it is plugged in, when it's not lit? What current goes through the bulb after it's lit?
  - (b) (2 points) What power does the bulb draw in both cases?
  - (c) (3 points) How many electrons pass through the bulb per second when it's lit?
  - (d) (3 points) A second light bulb is connected in series with the first one. How much power do both bulbs draw now?



3. The circuit shown above has resistors  $R_1 = 1.0 \Omega$ ,  $R_2 = 2.0 \Omega$ ,  $R_3 = 3.0 \Omega$ ,  $R_4 = 4.0 \Omega$ ,  $R_5 = 5.0 \Omega$ , and  $R_6 = 6.0 \Omega$  connected by perfectly conducting wires. The EMF  $V_7$  has a voltage across its terminals of  $V_7 = 12.0 \text{ V}$ . This circuit cannot be reduced to just parallel and series capacitors; you have to use Kirchhoff's rules to evaluate it.
- (2 points) Draw and label arrows for the six currents in the resistors in the diagram.
  - (4 points) There are four nodes in the above diagram. Select three of them and label them A, B, and C in the diagram. Using Kirchhoff's node rule and the currents you have drawn in part (a), write down the current equations for these three nodes.
  - (4 points) You need three more equations, so draw three Kirchhoff loops. Using Kirchhoff's loop rule, write down the three voltage equations for these loops.
  - (5 points) Solve the equations in parts (b) and (c) to find the currents in each of the resistors.